

A decorative graphic on the left side of the slide, consisting of a network of white lines and small circles on a blue gradient background, resembling a circuit board or a tree structure.


# THEVENIN EQUIVALENT

BY JAKE CLATTERBUCK

# OBJECTIVES

- To determine the Thevenin Equivalent of a given circuit
- To experimentally verify Thevenin's Theorem by building both circuits and observing their equivalence



# THE CIRCUIT

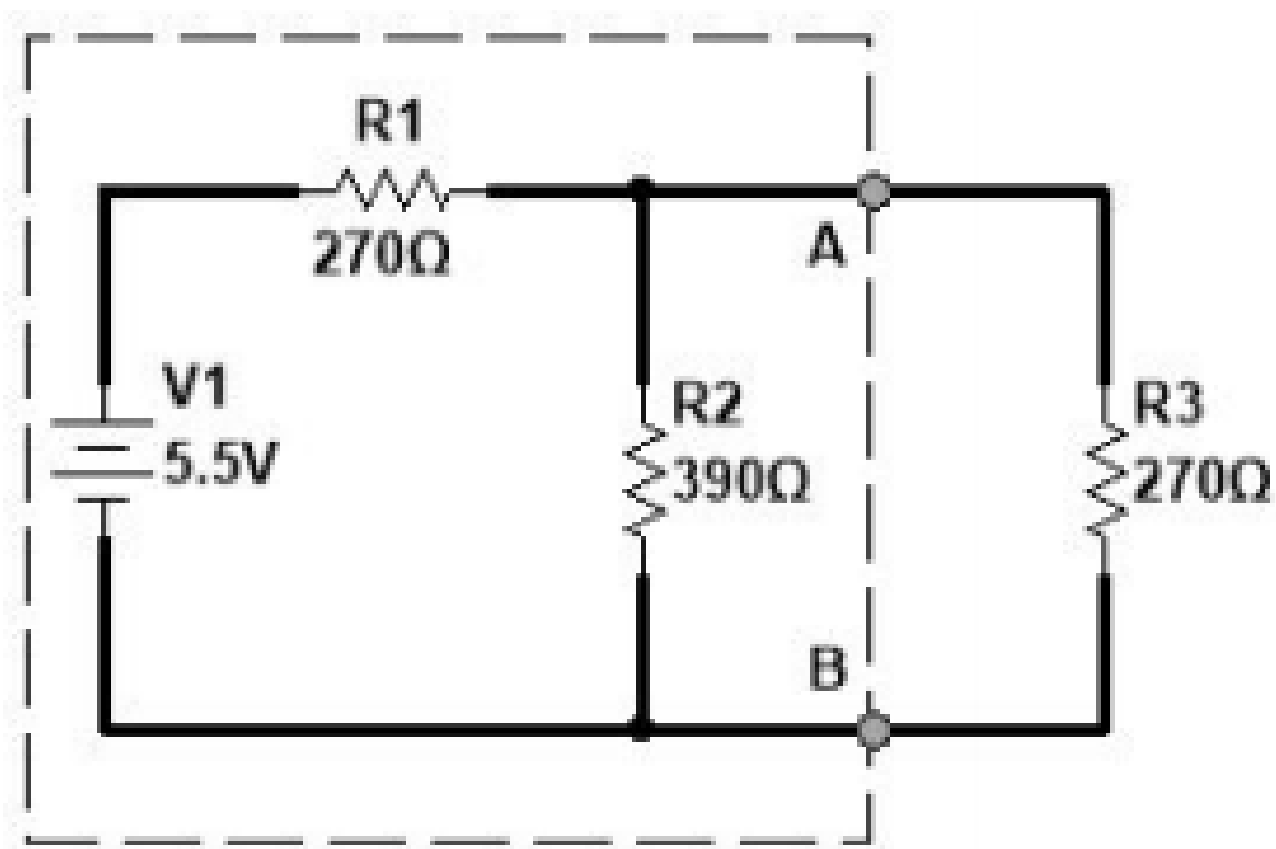

# VOLTAGE ACROSS LOAD RESISTOR

- Analytical: With the load resistor and 39k resistor in parallel ( $39k \parallel 27k = 15.95k$ ), the circuit becomes a voltage divider. The voltage across the combined resistors is equal to the voltage across the load.  
$$5.5V \cdot 16 / (16 + 27) = 2.04V$$

- Multisim: 2.04V
- Experimental: 2.045V

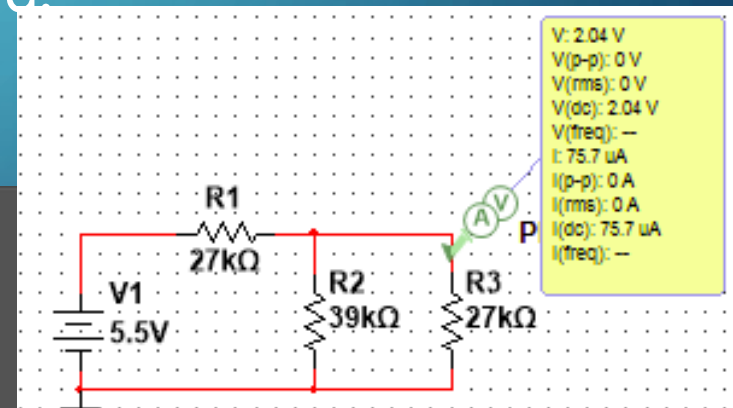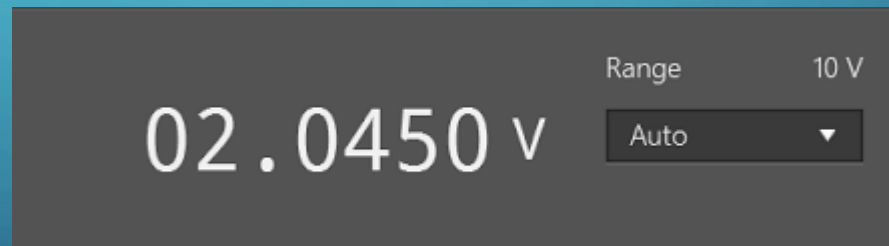

# CURRENT THROUGH LOAD RESISTOR

- Analytical: If voltage across the load is 2.04V, the load resistor is 27kOhms,  $V=IR$ ,  $I=V/R= 2.04/27000 = 75.6$  microAmps, or about .076mA


- MultiSim: 75.7 microAmps

- Experimental

00.0760 mA

Range


10 mA

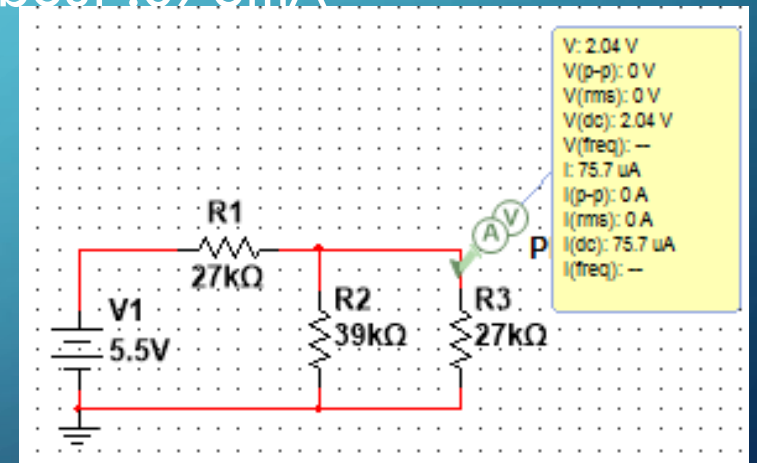


# OPEN CIRCUIT VOLTAGE

- Analytical: With an open circuit in place of the load, the circuit becomes a simple voltage divider.  $5.5 \times 39 / (39 + 27) = 3.25\text{V}$

- Multisim: 3.25V

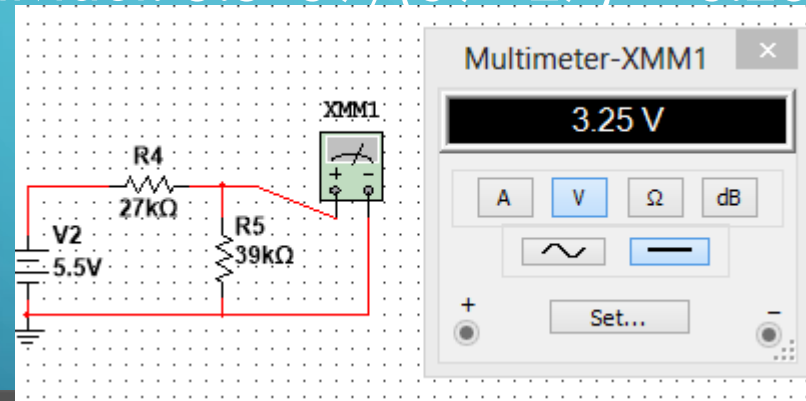


- Experimental:

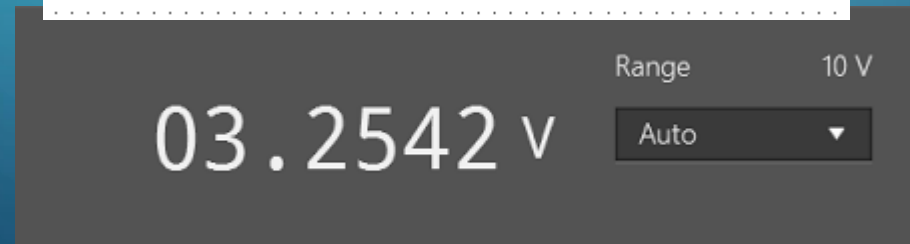

# THEVENIN RESISTANCE

- Using Method 2: The voltage source is replaced by a short circuit. The remaining circuit's equivalent resistance is then easily found as 2 parallel resistors.  $27 * 39 / (27 + 39) = 15.95 \text{k}\Omega$


# THEVENIN CIRCUIT

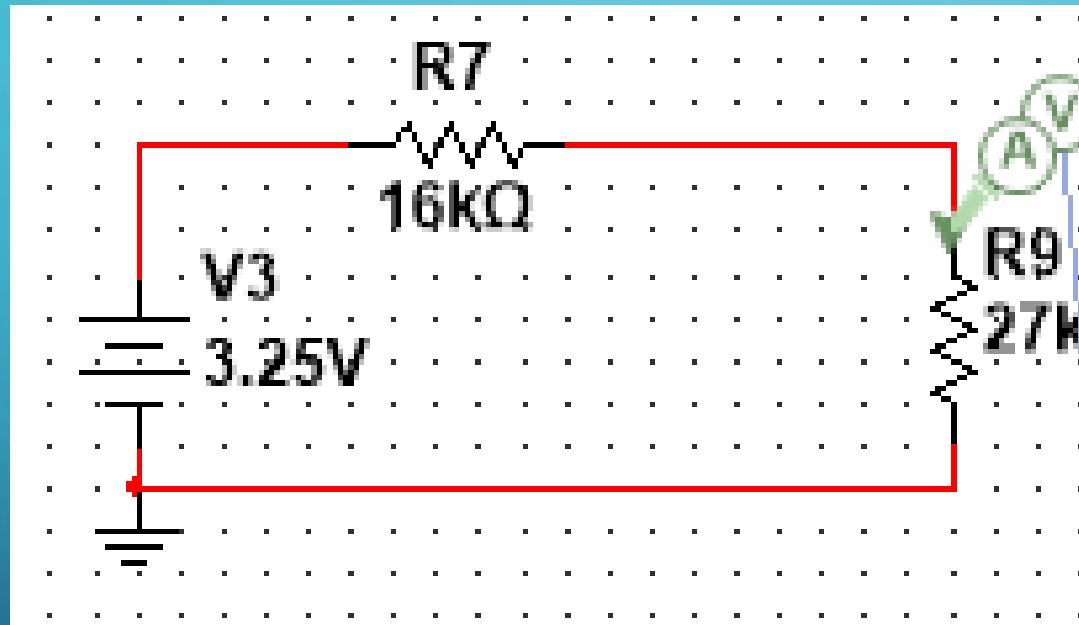




# EXPERIMENTAL VERIFICATION OF THEVENIN EQUIVALENT

- Voltage across load:

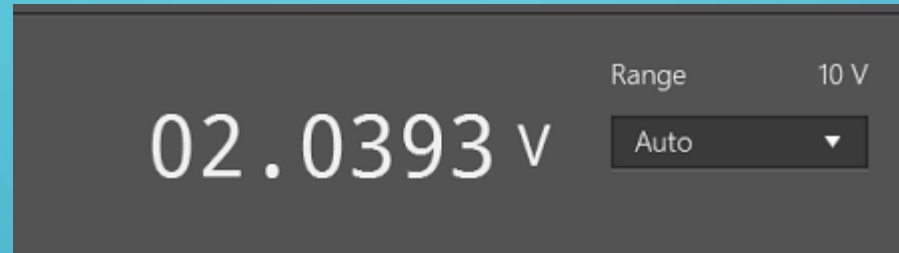

- Current through load:

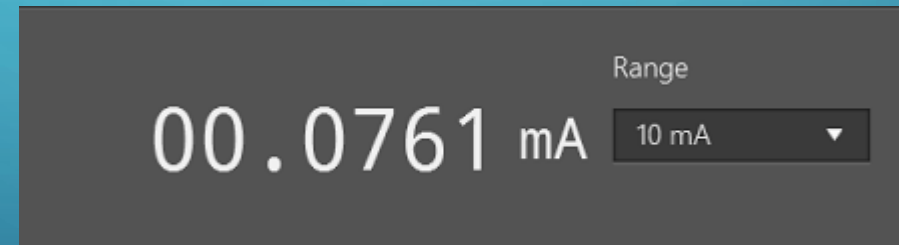

# CONCLUSION

- Thevenin's Theorem is shown to work, as the constructed thevenin equivalent circuit performs the same as the original circuit.