

A decorative graphic on the left side of the page consisting of white and light blue lines and circles, resembling a circuit board or a stylized tree structure, set against a blue gradient background.

WHEATSTONE BRIDGE

BY JAKE CLATTERBUCK

OBJECTIVES

- To learn about two-terminal resistive sensing devices such as the thermistor and photoresistor
- To learn about basic observation of sensor signals
- To gain experience working with the Wheatstone Bridge circuit


THERMISTOR

- Resistance of the element changes with heat (decreases with heat)

- Room temperature:




- Squeezed:

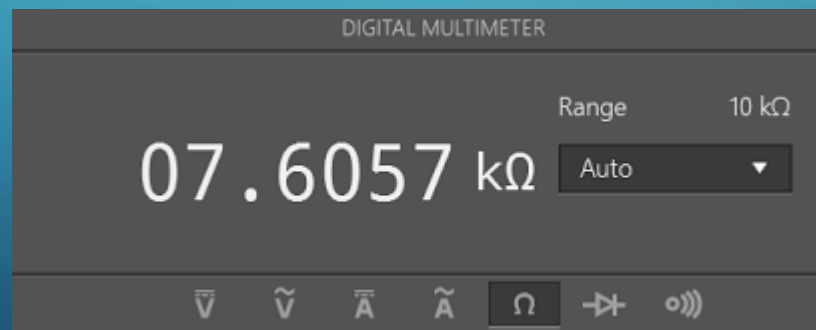


PHOTORESISTOR

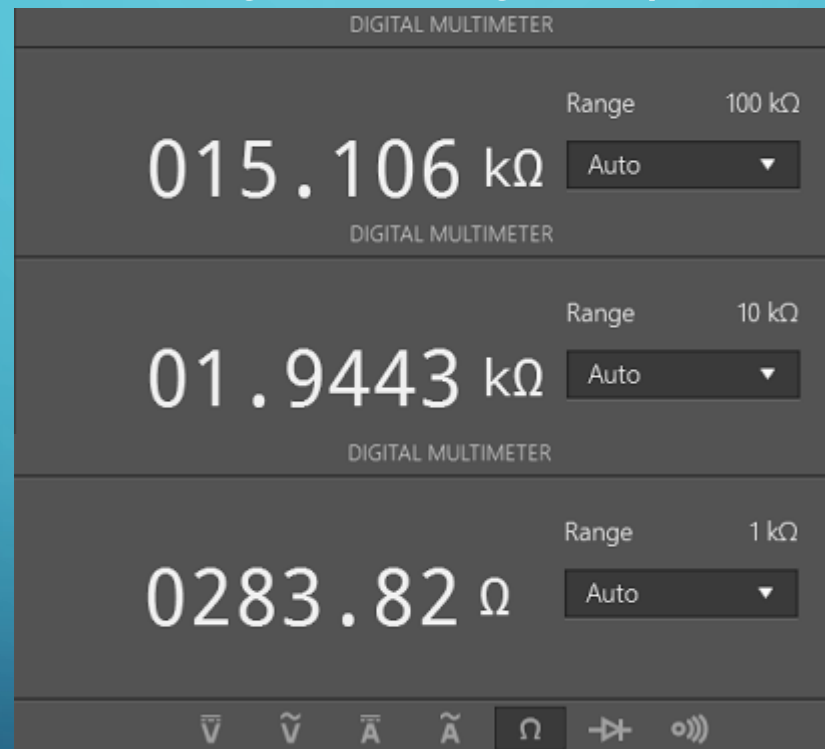- Resistance of the element changes with light exposure (decreases with light)
- Covered in darkness:
 - Room lighting:
 - Flashlight shining:



VOLTAGE DIVIDER

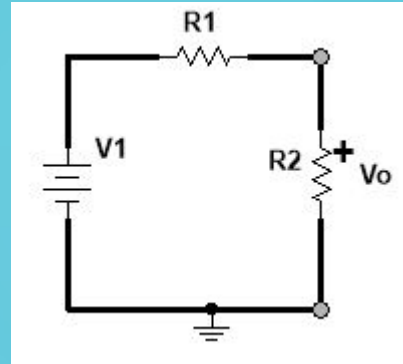

- A voltage divider was set up to test both resistors in a circuit
- V1 was set to 5 volts
- For R1 a 10k ohm resistor was used
- R2 was either the photoresistor or the thermistor
- V_o measurements are as follows

VOLTAGE DIVIDER VOLTAGE OUTPUTS

- Thermistor Room Temperature:



- Thermistor Squeezed:



- $P=IV$, $V=5$, $I=V_o/R$
- Power calculated as $V_o \cdot 5V/R$: $(2.46 \cdot 5)/10485 = 1.17\text{mW} < .125\text{W}$
- Power calculated as $V_o \cdot 5/R$: $(2.06 \cdot 5)/7606 = 1.35\text{mW} < .125\text{W}$

VOLTAGE DIVIDER VOLTAGE OUTPUTS

- Photoresistor covered:



- Photoresistor room light:




- Photoresistor flashlight:



- Power calculated as previously shown respectively: 1.0mW, 2.0mW, 1.5mW


WHEATSTONE BRIDGE

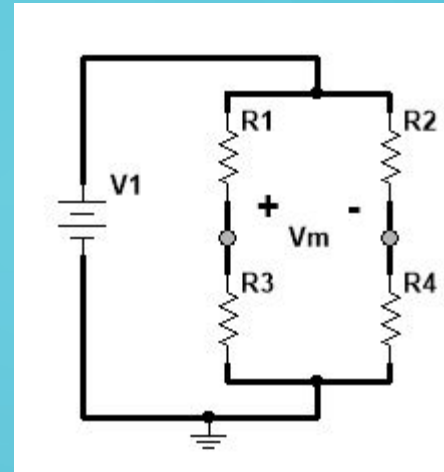

- R1 is either the photoresistor or thermistor
- R2 is a potentiometer
- R3 and R4 are both either 10k or 4.7k ohm resistors
- With the sensing resistor in its natural room state, the potentiometer was adjusted until $V_m = 0$. The sensing element's environment was then changed to see the effect on V_m without changing the potentiometer.


WHEATSTONE THERMISTOR TRIALS

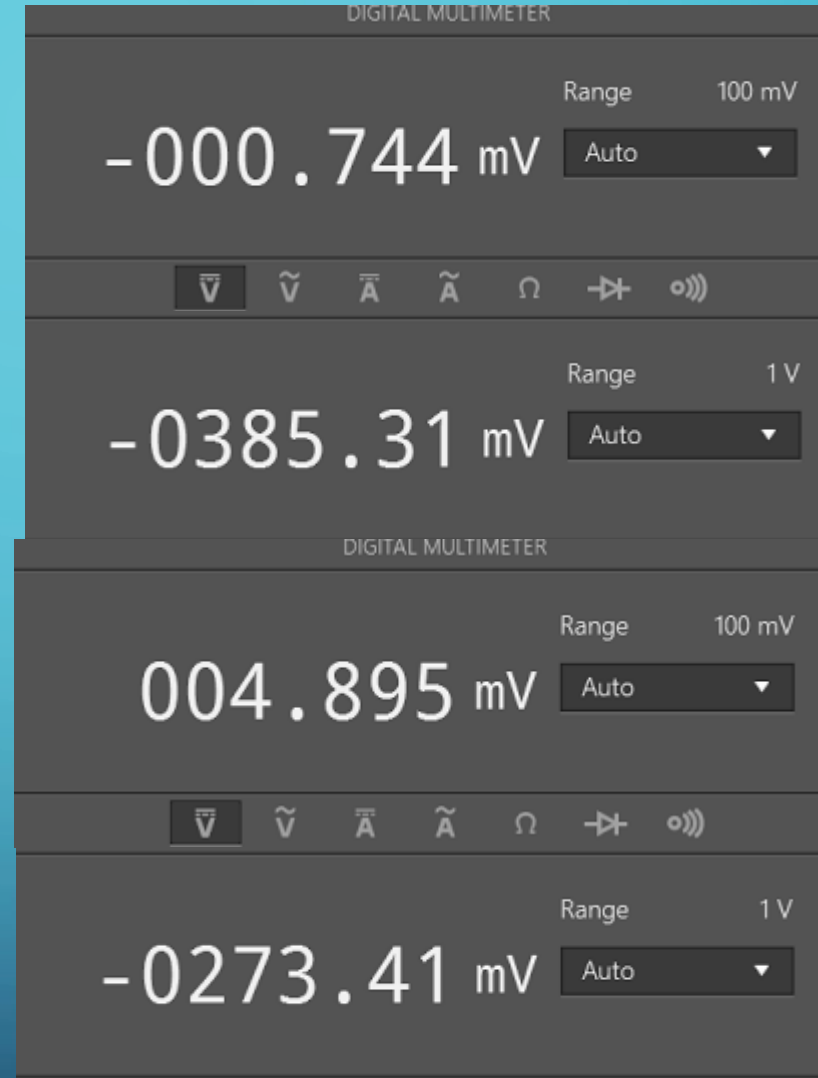- Room temperature with 10k
- Squeezed temperature with 10k
- Room temperature with 4.7k
- Squeezed temperature with 4.7k




WHEATSTONE POTENTIOMETER TRIALS

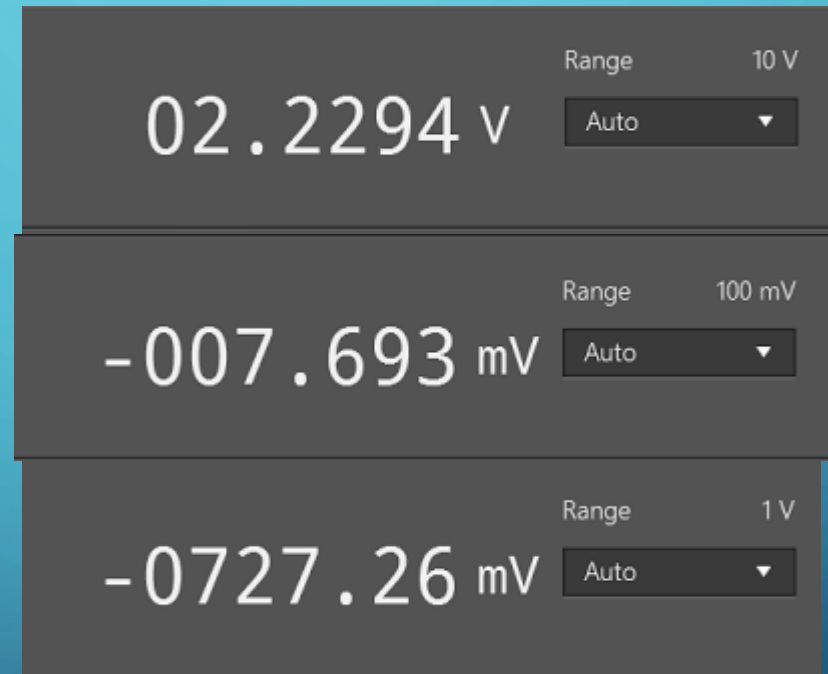- Covered lighting with 10k
- Room lighting with 10k
- Flashlight with 10k



WHEATSTONE POTENTIOMETER TRIALS

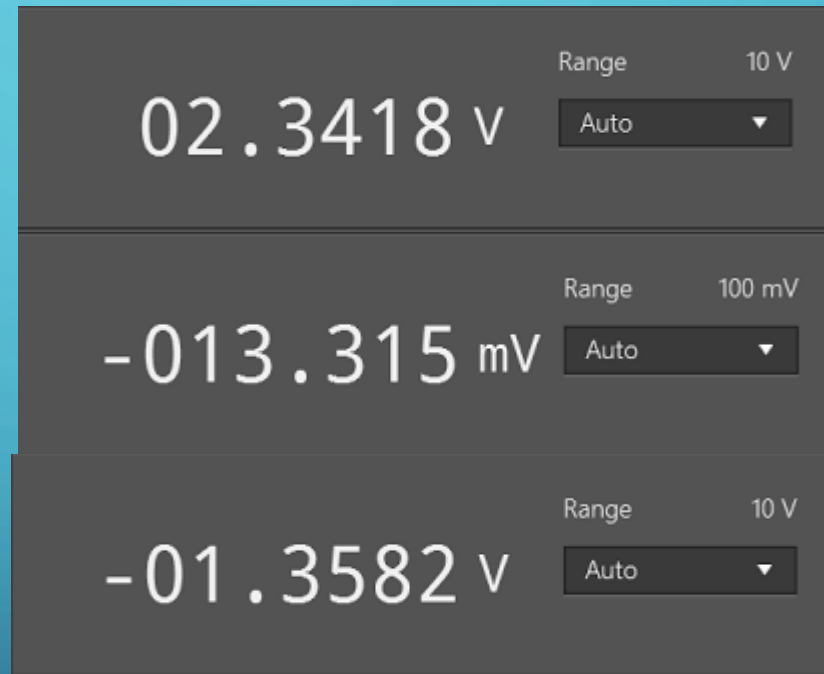- Covered lighting with 4.7k
- Room lighting with 4.7k
- Flashlight with 4.7k



CONCLUSIONS

- When the resistance of the element changes, the wheatstone voltage swings one way or the other with the potentiometer at a set value.
- The wheatstone bridge can therefor be used to sense changes in a resistive element.